 


# LSIC Project



**Andrei LAZAROV**

CTI En, Year 3

1<sup>st</sup> semester

2022-2023

# Table of contents

<b>Overview</b>	<b>3</b>
<b>Project description</b>	<b>3</b>
<b>Milestones</b>	<b>3</b>
<b>Schematic</b>	<b>4</b>
<b>Files</b>	<b>5</b>
1. top_module.v	5
2. timer.v	6
3. seven_seg.v	8
4. fdfs.ucf	10

# Overview

At the LSIC laboratory meetings, we learned to program an FPGA board by writing Verilog code. The trainer board was a [Digilent Nexys 2](#).

## Project description

After uploading the generated programming file, the board will start the counter and display the seconds passed:

- in **binary** with the 8 LEDs
- in **hexadecimal** on the 4-digit seven-segment display

The user has 3 controls available:


1. **Start** - first switch (R17)
2. **Stop** - second switch (N17)
3. **Pause** - third switch (L13)

To send a control signal - toggle the switch on and back off. (use them as push buttons)

## Milestones

- Blinking an LED  
Getting used to the board and the tools;
- Time measurement  
Count clock ticks and store seconds passed based on frequency;  
Display time in binary;
- 7-segment display output  
Display time in hexadecimal;
- States / opcodes  
Start, stop and pause the timer with buttons/switches;
- Memories
- Wishbone

# Schematic

 

# Files

The code is written in 4 files:

## 1. top\_module.v

The top level module - instantiates the other two modules.

```
`timescale 1ns / 1ps

module top_module(
    input clk,
    input [2:0] ctrl,
    output [15:0] sec,
    output [3:0] enable,
    output [6:0] sev
);

    timer t (
        .clk (clk),
        .ctrl (ctrl),
        .sec (sec)
    );

    seven_seg ss (
        .clk (clk),
        .sec (sec),
        .sev (sev),
        .enable (enable)
    );

endmodule
```

## 2. timer.v

Contains timer module - responsible with time measurement and states

```
`timescale 1ns / 1ps

`define ST_IDLE    3'b000    //idle
`define ST_START   3'b001    //start
`define ST_STOP    3'b010    //stop
`define ST_PAUSE   3'b100    //pause

module timer(
    input          clk,
    input  [2:0]   ctrl,
    output [15:0]  sec
);

    reg [2:0] state_reg, state_nxt;
    reg [31:0] cnt_reg, cnt_nxt;
    reg [15:0] sec_reg, sec_nxt;

    assign sec = sec_reg;

    always @ (posedge clk) begin

        cnt_reg <= cnt_nxt;
        sec_reg <= sec_nxt;
        state_reg <= state_nxt;
    end

    always @ (*) begin

        cnt_nxt = cnt_reg;
        sec_nxt = sec_reg;
        state_nxt = state_reg;

        case (state_reg)

            `ST_IDLE: begin

                if (ctrl[0]==1) state_nxt = `ST_START;
                else if (ctrl[1]==1) state_nxt = `ST_STOP;
                else if (ctrl[2]==1) state_nxt = `ST_PAUSE;
            end

        endcase
    end
endmodule
```

```

`ST_START: begin

    cnt_nxt = cnt_reg + 1;

    if (cnt_reg == 49_999_999) begin
        sec_nxt = sec_reg + 1;
        cnt_nxt = 0;
    end

    if (ctrl[0]==1) state_nxt = `ST_START;
    else if (ctrl[1]==1) state_nxt = `ST_STOP;
    else if (ctrl[2]==1) state_nxt = `ST_PAUSE;
end

`ST_STOP: begin

    cnt_nxt = 0;
    sec_nxt = 0;
    if (ctrl[0]==1) state_nxt = `ST_START;
    else if (ctrl[1]==1) state_nxt = `ST_STOP;
    else if (ctrl[2]==1) state_nxt = `ST_PAUSE;
end

`ST_PAUSE: begin

    cnt_nxt = cnt_reg;
    if (ctrl[0]==1) state_nxt = `ST_START;
    else if (ctrl[1]==1) state_nxt = `ST_STOP;
    else if (ctrl[2]==1) state_nxt = `ST_PAUSE;
end
endcase
end
endmodule

```

### 3. seven\_seg.v

Contains seven\_seg module - writes the output to the seven segment display

```
module seven_seg(  
    input          clk,  
    input [15:0]    sec,  
    output [3:0]    enable,  
    output [6:0]    sev  
);  
  
    reg [3:0] enable_reg;  
    assign enable = enable_reg;  
  
    reg [6:0] sev_reg;  
    assign sev = sev_reg;  
  
    reg [3:0] hex_digit;  
  
    reg [1:0] select_digit_reg, select_digit_nxt;  
    reg [31:0] cnt_reg, cnt_nxt;  
  
    always @ (posedge clk) begin  
        select_digit_reg <= select_digit_nxt;  
        cnt_reg <= cnt_nxt;  
    end  
  
    always @ (*) begin  
  
        if (select_digit_reg == 3 & cnt_reg == 199_999)  
            select_digit_nxt = 0;  
        else if (cnt_reg == 199_999)  
            select_digit_nxt = select_digit_reg + 1;  
        else  
            select_digit_nxt = select_digit_reg;  
  
        cnt_nxt = cnt_reg + 1;  
  
        if (cnt_reg == 199_999)  
            cnt_nxt = 0;  
  
        case (select_digit_reg)  
            0 : begin  
                enable_reg = 4'b1110;  
                hex_digit = sec[3:0];  
            end  
  
        end  
    end  
end
```



```

        1 : begin
            enable_reg = 4'b1101;
            hex_digit = sec[7:4];
        end
        2 : begin
            enable_reg = 4'b1011;
            hex_digit = sec[11:8];
        end
        3 : begin
            enable_reg = 4'b0111;
            hex_digit = sec[15:12];
        end
    endcase
end

always @(*)
    case (hex_digit)
        4'b0001 : sev_reg = 7'b1111001; // 1
        4'b0010 : sev_reg = 7'b0100100; // 2
        4'b0011 : sev_reg = 7'b0110000; // 3
        4'b0100 : sev_reg = 7'b0011001; // 4
        4'b0101 : sev_reg = 7'b0010010; // 5
        4'b0110 : sev_reg = 7'b0000010; // 6
        4'b0111 : sev_reg = 7'b1111000; // 7
        4'b1000 : sev_reg = 7'b0000000; // 8
        4'b1001 : sev_reg = 7'b0010000; // 9
        4'b1010 : sev_reg = 7'b0001000; // A
        4'b1011 : sev_reg = 7'b0000011; // b
        4'b1100 : sev_reg = 7'b1000110; // C
        4'b1101 : sev_reg = 7'b0100001; // d
        4'b1110 : sev_reg = 7'b0000110; // E
        4'b1111 : sev_reg = 7'b0001110; // F
        default : sev_reg = 7'b1000000; // 0
    endcase
endmodule

```

## 4. fdsf.ucf

User constraint file - maps inputs and outputs to physical pins.

- The 8 LEDs display the seconds passed in binary (LED on = 1, off = 0) from the sec output.
- *clk* gets the real clock signal
- *sev* is mapped to the seven segments of a digit
- *enable* selects the digit
- *ctrl* gets the input switches states

```
NET "sec[7]" LOC = "R4";
NET "sec[6]" LOC = "F4";
NET "sec[5]" LOC = "P15";
NET "sec[4]" LOC = "E17";
NET "sec[3]" LOC = "K14";
NET "sec[2]" LOC = "K15";
NET "sec[1]" LOC = "J15";
NET "sec[0]" LOC = "J14";

NET "clk" LOC = "B8";

NET "sev[0]" LOC = "L18"; //a
NET "sev[1]" LOC = "F18"; //b
NET "sev[2]" LOC = "D17"; //c
NET "sev[3]" LOC = "D16"; //d
NET "sev[4]" LOC = "G14"; //e
NET "sev[5]" LOC = "J17"; //f
NET "sev[6]" LOC = "H14"; //g

NET "enable[0]" LOC = "F17"; //AN0
NET "enable[1]" LOC = "H17"; //AN1
NET "enable[2]" LOC = "C18"; //AN2
NET "enable[3]" LOC = "F15"; //AN3

NET "ctrl[0]" LOC = "R17"; //START
NET "ctrl[1]" LOC = "N17"; //STOP
NET "ctrl[2]" LOC = "L13"; //PAUSE
```